



**Vidyavardhini's College of Engineering and Technology**  
**Department of Artificial Intelligence & Data Science**

<b>Experiment No.4</b>
Aim: Study of flip flip IC
Name: Parth Sadanand Gawad
Roll no: 68
Date of Performance: 9/8/2024
Date of Submission: 16/8/2024



# Vidyavardhini's College of Engineering and Technology

## Department of Artificial Intelligence & Data Science

---

**Aim** - Study of flip flop IC

**Objective** - The primary objective of this experiment is to study the behavior and functionality of flip-flop Integrated Circuits (ICs). Specifically, the goals are:

1. To understand the operation of different types of flip-flops (e.g., SR, JK, D, and T flip-flops).
2. To observe how flip-flops store and transfer binary data.
3. To analyze the timing diagrams and characteristic behaviors of flip-flop circuits.

**Components required - Flip-Flop ICs** (e.g., 7473, 7474, 4013, 4027)

- SR Flip-Flop IC: 7473
- D Flip-Flop IC: 7474
- JK Flip-Flop IC: 7476
- T Flip-Flop IC: 4013

**Breadboard** for circuit assembly

**Connecting Wires** for circuit connections

**Power Supply** (5V DC)

**Oscilloscope** for observing timing diagrams

**Logic Probe** or **LEDs** to indicate output states

**Switches** for manual input control

**Resistors** and **Capacitors** (for optional timing and filtering)

**Clock Generator** (if not using an internal clock source)

**Theory -Flip-Flops:** A flip-flop is a digital electronic circuit used to store one bit of data. It is a basic building block of sequential logic circuits and has two stable states, representing binary 0 and 1. Flip-flops are used in a variety of applications including memory storage, data transfer, and frequency division.

### Types of Flip-Flops:

1. **SR Flip-Flop (Set-Reset):** The SR flip-flop has two inputs, Set (S) and Reset (R), and two outputs, Q and  $\overline{Q}$ . It is used to store a single bit of data and can be set or reset by the inputs. The behavior of the SR flip-flop is defined by the following conditions:
  - S = 1, R = 0: Q = 1
  - S = 0, R = 1: Q = 0
  - S = 0, R = 0: Q remains unchanged
  - S = 1, R = 1: This condition is typically invalid or results in an indeterminate state.



# Vidyavardhini's College of Engineering and Technology

## Department of Artificial Intelligence & Data Science

---

2. **JK Flip-Flop:** The JK flip-flop is a more versatile version of the SR flip-flop, where both inputs (J and K) control the state transitions. It can toggle its state, hold its state, or reset based on the input conditions:
  - $J = 0, K = 0$ : No change
  - $J = 0, K = 1$ : Reset ( $Q = 0$ )
  - $J = 1, K = 0$ : Set ( $Q = 1$ )
  - $J = 1, K = 1$ : Toggle state
3. **D Flip-Flop (Data or Delay):** The D flip-flop captures the value of the data input (D) on the edge of the clock pulse and transfers it to the output (Q). It is used to eliminate the indeterminate state problem of the SR flip-flop:
  - On the rising edge of the clock, Q takes the value of D.
4. **T Flip-Flop (Toggle):** The T flip-flop toggles its output on every clock pulse if the T input is high. It is often used as a frequency divider:
  - $T = 1$ : Q toggles
  - $T = 0$ : Q remains unchanged

**Conclusion** -The experiment successfully illustrated how each type of flip-flop operates, their respective timing diagrams, and their practical applications in digital circuits. Understanding these flip-flops provides a solid foundation for designing and analyzing more complex sequential logic systems in digital electronics.